

TEAM MAVERICKS

ADITYA RAJ & ARYANSH KUMAR

COMMNET PROBLEM STATEMENT 1

Problem Statement :

We are required to design a two stage miller-compensated op-amp with a capacitive load. A typical two stage op-amp looks like:

 


Figure 1: NMOS Two Stage op amp


Specifications	Value
DC Gain	2000
Input Common Mode Range	0.7 V to 1.6 V
Phase margin	> 60 degrees
Capacitive load (C_L)	5 pF
Gain-bandwidth (GBW) product	50 MHz

$$V_{th}(\text{for nmos}) = 0.7 \pm 0.15V, \lambda = 0.04 \text{ and } U_n C_{ox} = 100 \mu A/V^2 \pm 10\%$$

$$V_{th}(\text{for pmos}) = -0.7 \pm 0.15, \lambda = 0.05, U_p C_{ox} = 50 \mu A/V^2 \pm 10\%$$

Introduction to Two Stage OpAmp :

Operational amplifiers (opamp) are essential components of analog system design. Integrated circuit design, as well as board level design, often uses operational amplifiers. This component is basically a high gain voltage amplifier used in many analog systems such as filters, regulators and function generators. This rudimentary device is also used to create buffers, logarithmic amplifiers and instrumentation amplifiers. Op Amps can also function as simple comparators. Knowledge of operational amplifier functionality and design is important in analog design.

 


The operational amplifier functions as a voltage amplifier. The relationship between the input and output voltage is given by:

$$V_o = A_{vo} (V_i^+ - V_i^-)$$

The simplest operational amplifier is the simple differential amplifier studied earlier. This amplifier can be improved by adding a second stage as an inverting amplifier with a current source load. The two stage amplifier shown in Figure 1 (on pg no. 1) is referred to as a Miller compensated Opamp.

There was a need for two-stage operational amplifiers because they can provide high gain and high output swing in comparison to single Op Amp.


The two-stage amplifier can be modeled as a cascade of two amplifiers, as illustrated in Figure 8-4. The first stage is a differential amplifier, which produces an amplified version of the difference in input signals. This stage determines the CMRR, slew rate and other performance specifications determined by the differential amplifier. The second stage is an inverting amplifier. The purpose of this stage is to provide a large voltage gain. The gain stage and the input stage create two poles, which affect the stability of the feedback system. Usually some form of compensation is required to assure the amplifier is stable at unity gain. The technique used here is called Miller Compensation. Additional gain stages can be employed to increase the gain, but this degrades stability and requires complex compensation techniques.

 

What is Miller Compensation :

Miller compensation is a technique for stabilizing op-amps by means of a capacitance C_f connected in *negative-feedback fashion* across one of the *internal gain stages*, typically the second stage.

 The addition of the compensation capacitor C_c caused the poles to split. One pole moved closer to the origin, while the other pole moved away from the origin. This compensation technique is called "pole splitting". The pole-zero plot of this transfer function is illustrated in Figure 8-8.




Important formulas :

$$GBW = gm_1 / C_c$$

$$p_1 = 1 / (gm_2 \times R_1 \times R_2 \times C_c)$$

$$p_2 = gm_2 / C_L$$

$$Zero = gm_2 / C_c$$

 

Design Procedure (Using Miller Compensation) :

Step 1 :

- Evaluation of C_c from C_L To obtain a phase margin of 60° , it is required that the compensating capacitor C_c satisfy this following condition, i.e

$$C_c \geq 0.22 \times C_L$$

Step 2 :

- Evaluation of I_o from slew rate The slew rate of 2-stage Miller compensated OTA is given by,

$$I_{D5} = SR \times C_c$$

Step 3 :

- Evaluation of $(w/l)_{3,4}$

$$(w/l)_{3,4} = I_{D5} / (U_p C_{ox} \times (V_{dd} - |V_{th3(max)}| - V_{in(max)} + V_{th1(min)})^2)$$

Step 4 :

- Evaluation of gm_1 We have,

$$gm_1 = GBW \times 2\pi \times C_c$$

- Now Evaluation of $(w/l)_{1,2}$

$$(w/l)_{1,2} = (gm_1)^2 / (U_n C_{ox} \times I_{D5})$$

Step 5 :

- Calculation of $V_{D5(sat)}$

$$V_{D5(sat)} = V_{in(min)} - V_{ss} - V_{th1(max)} - \sqrt{I_{D5} / (U_n C_{ox} \times (w/l)_{1,2})}$$

- Evaluation of $(w/l)_5$

$$(w/l)_5 = (2 \times I_{D5}) / (U_n C_{ox} \times V_{D5(sat)}^2)$$

$(w/l)_5 = (w/l)_8$; Since they form a current mirror circuit

Step 6 :

- Evaluation of gm_6

$$gm_6 \geq 10 \times gm_1$$

Select gm_6 from here then,

- Evaluation of gm_4

$$gm_4 = \sqrt{I_{D5} \times U_p C_{ox} \times (w/l)_{3,4}}$$

- Evaluation of $(w/l)_6$

$$(w/l)_6 = (w/l)_{3,4} \times (gm_6 / gm_4)$$

Step 7 :

- Evaluation of I_{D6}

$$I_{D6} = (gm_6)^2 / (2 \times U_p C_{ox} \times (w/l)_6)$$

$$I_{D7} = I_{D6}$$

Step 8 :

- Evaluation of $(w/l)_7$

$$(w/l)_7 = (w/l)_5 \times (I_{D7} / I_{D5})$$

Code for parameter calculations :

```

C++ commnet.cpp > main()
1  #include<bits/stdc++.h>
2  using namespace std;
3  int main(){
4      float icmrpos,icmrneg,vdd,vss;
5      // cout<<"enter vdd"<<endl;
6      cin>>vdd;
7      // cout<<"enter vss"<<endl;
8      cin>>vss;
9      float sr;
10     // cout<<"enter sr"<<endl;
11     cin>>sr;
12     float cc;
13     // cout<<"enter cc"<<endl;
14     cin>>cc;

```

>>As it was tedious to calculate manually again and again so We have written, C++ code for calculating parameters by taking user input V_{dd} , V_{ss} , Slew Rate, and Cc.

```

C++ commnet.cpp > main()
3  int main(){
15     if(cc>1.1){
16         float id5=sr*cc;
17         cout<<"id5 = "<<id5<<"micro"<<endl;
18         float r3=(id5/(50*((vdd-1.9)*(vdd-1.9))));
19         // int r4=r3;
20         cout<<"r3 = "<<r3<<endl;
21         // cout<<"r4 = "<<r4<<endl;
22         float gm1=314.159*cc;
23         cout<<"gm1 = "<<gm1<<" micro"<<endl;
24         int r1=ceil((gm1*gm1)/(100*id5));
25         cout<<"r1 = "<<r1<<endl;
26         int r2=r1;
27         float vd5sat=(-0.15-vss-sqrt(id5/(100*r1)));
28         cout<<"vd5sat = "<<vd5sat<<endl;
29         int r5=ceil((2*id5)/(100*vd5sat*vd5sat));
30         cout<<"r5 = "<<r5<<endl;
31         int gm6=ceil(10*gm1);
32         cout<<"gm6 = "<<gm6<<"micro"<<endl;
33         float gm4=sqrt(id5*50*r3);
34         cout<<"gm4 = "<<gm4<<"micro"<<endl;
35         int r6=ceil((r3*gm6)/(gm4));
36         cout<<"r6 = "<<r6<<endl;
37         float id6=(gm6*gm6)/(100*r6);
38         cout<<"id6 = "<<id6<<"micro"<<endl;
39         int r7=ceil((id6*r5)/id5);
40         cout<<"r7 = "<<r7<<endl;
41         float gain=(2*gm1*gm6)/(id5*id6*0.09*0.09);

```

>>Defining all parameters with given formulas and printing the calculated values .

>>Gain as Output

```

43         cout<<"gain = "<<gain<<endl;
44     }
45     return 0;
46
47 }

```

For input $V_{dd} = 2.5\text{v}$

$V_{ss} = -1.5\text{v}$

Slew Rate = 32 v/us

$C_c = 1.4\text{pf}$ (i.e greater than 1.1pf as from step 1 as C_L is 5 pf)

Output from given code is:

Received Output:

Copy

$id5 = 44.8\text{micro}$

$r3 = 2.48889$

$gm1 = 439.823\text{ micro}$

$r1 = 44$

$vd5sat = 1.24909$

$r5 = 1$

$gm6 = 4399\text{micro}$

$gm4 = 74.6667\text{micro}$

$r6 = 147$

$id6 = 1316\text{micro}$

$r7 = 30$

$gain = 8102.94$

I_{D5} = Drain current of M_5

$r_3 = (w/l)_{3,4}$

gm_1 = Transconductance of M_1

$r_1 = (w/l)_{1,2}$

$V_{D5(sat)}$ = Voltage required for M_5 to remain in saturation

$r_5 = (w/l)_{5,8}$

gm_6 = Transconductance of M_6

gm_4 = Transconductance of M_4

$r_6 = (w/l)_6$

I_{D6} = Drain current of M_6

$r_7 = (w/l)_7$

Gain = Calculated gain at particular frequency

Calculated Parameters:-

Specifications	Value	Width
$(w/l)_{1,2}$	44	22u
$(w/l)_{3,4}$	2.5	1245n
$(w/l)_{5,8}$	1	500n
$(w/l)_6$	147	73.5u
$(w/l)_7$	30	15u
I_{D5}	44.8 micro	
C_c	1.4 pf	

Value of L for all mosfets are taken as 500 nm and value of width is calculated accordingly.


V_{in-}
 V_3
 0.7
 V_4
 $\text{SINE}(0 \text{ } -0.01\text{m } 100)$
 $\text{AC } -100\text{m}$
 V_{in+}
 V_2
 0.7
 V_5
 $\text{SINE}(0 \text{ } 0.01\text{m } 100)$
 $\text{AC } 100\text{m}$
 V_{ss}
 V_6
 -1.5
 I_b
 44.8μ
 V_{in-}
 M_1
 NMOS
 M_2
 NMOS
 V_{in+}
 M_3
 PMOS
 M_4
 PMOS
 M_5
 NMOS
 M_6
 PMOS
 M_7
 NMOS
 M_8
 NMOS
 V_{dd}
 2.5
 CC
 1.4p
 CL
 5p
 V_{out}
 15V
 V_{ss}
 $.model \text{ PMOS PMOS (kp=50u vt0=-0.7 lambda=0.05)}$
 $.model \text{ NMOS NMOS (kp=100u vt0=0.7 lambda=0.04)}$
 $.ac \text{ dec } 10 \text{ } 1 \text{ } 10\text{G}$

DC operating point :


--- Operating Point ---			Ib (M5) :	-1.41205e-12	device_current
			Is (M5) :	-4.44376e-05	device_current
			Id (M8) :	4.48e-05	device_current
V(n001) :	2.5	voltage	Ig (M8) :	0	device_current
V(n007) :	0.117364	voltage	Ib (M8) :	-1.62736e-12	device_current
V(vout) :	0.436008	voltage	Is (M8) :	-4.48e-05	device_current
V(n004) :	1.2208	voltage	Id (M7) :	0.00136009	device_current
V(vin+) :	0.7	voltage	Ig (M7) :	0	device_current
V(n005) :	0	voltage	Ib (M7) :	-1.94601e-12	device_current
V(vin-) :	0.7	voltage	Is (M7) :	-0.00136009	device_current
V(n002) :	0	voltage	Id (M4) :	-2.22188e-05	device_current
V(n003) :	1.2208	voltage	Ig (M4) :	-0	device_current
V(n006) :	-0.0979459	voltage	Ib (M4) :	1.2892e-12	device_current
V(vss) :	-1.5	voltage	Is (M4) :	2.22188e-05	device_current
Id (M1) :	2.22188e-05	device_current	Id (M6) :	-0.00136009	device_current
Ig (M1) :	0	device_current	Ig (M6) :	-0	device_current
Ib (M1) :	-1.32875e-12	device_current	Ib (M6) :	2.07399e-12	device_current
Is (M1) :	-2.22188e-05	device_current	Is (M6) :	0.00136009	device_current
Id (M2) :	2.22188e-05	device_current	Id (M3) :	-2.22188e-05	device_current
Ig (M2) :	0	device_current	Ig (M3) :	-0	device_current
Ib (M2) :	-1.32875e-12	device_current	Ib (M3) :	1.2892e-12	device_current
Is (M2) :	-2.22188e-05	device_current	Is (M3) :	2.22188e-05	device_current
Id (M5) :	4.44376e-05	device_current	I (Cc) :	-1.09871e-24	device_current
Ig (M5) :	0	device_current	I (Cl) :	-2.18004e-24	device_current
Ib (M5) :	-1.41205e-12	device_current	I (Ib) :	4.48e-05	device_current
Is (M5) :	-4.44376e-05	device_current	I (Vdd) :	-0.00144933	device_current
Id (M8) :	4.48e-05	device_current	I (V2) :	0	device_current
Ig (M8) :	0	device_current	I (V3) :	0	device_current
			I (V4) :	0	device_current
			I (V5) :	0	device_current
			I (V6) :	0.00144933	device_current

Bode plot :

At Input common dc voltage 0.7 Volts

 

At Input common dc voltage 1.6 Volts

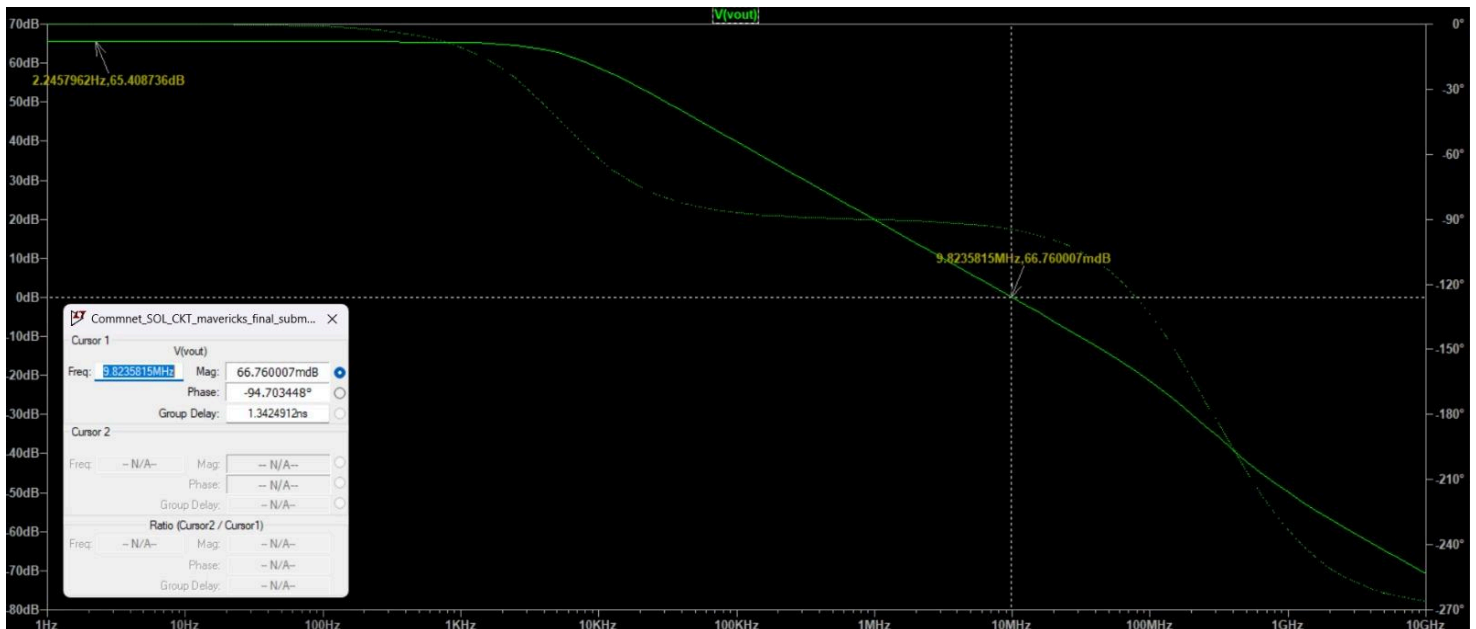

Error :

Calculated Gain (at particular frequency) :- 78.17 dB

DC Gain (simulation):- 66.01 dB(for 0.7 volts) and 65.408 dB(for 1.6 volts)

Absolute Error = 12.16 dB (for 0.7 volts) and 12.762 dB(for 1.6 volts)

Specifications(LTSpice)	Value(At 0.7v)	Value(At 1.6v)
DC Gain	1997.56	1862.08
Phase Margin	85.23	85.297
Gain Bandwidth Product	9.98 MHz	9.82 MHz

As we can clearly see that our gain bandwidth product is very far away from expected (50 Mhz). Hence we try to decrease C_c as our GBW product is inversely proportional to C_c (as seen from table below). But after repeated simulations and calculations we see that our gain bandwidth remains nearly 10 Mhz for decreasing C_c value to 1.2pf.

So now we further decrease it below 1.1pf to see the output results.

And after the simulation at somewhat lower values of C_c also we see that our phase margin is ($>60^\circ$).

We have not increased the value of current I_5 because it will change our DC gain.


We have to compromise any value between Gain and Gain Bandwidth product as there is tradeoff between Gain and Gain Bandwidth product. The below circuit is realized only on the simulation basis.

Dependencies of device performance on various parameters

		Drain Current		M1 and M2		M3 and M4		Inverter	Inverter Load	Comp. Cap..
		I_5	I_7	W/L	L	W	L	W_6/L_6	W_7/L_7	C_c
Increase Gain	DC	(↓)1/2	(↓)1/2	(↑)1/2	↑	↑		(↑)1/2	↑	
Increase GB		(↑)1/2		(↑)1/2						↓
Increase RHP Zero	RHP		(↑)1/2					(↑)1/2		↓
Increase Slew Rate	Slew	↑								↓
Increase C_L										↓

Image source - Allen and Holberg - CMOS Analog Circuit Design

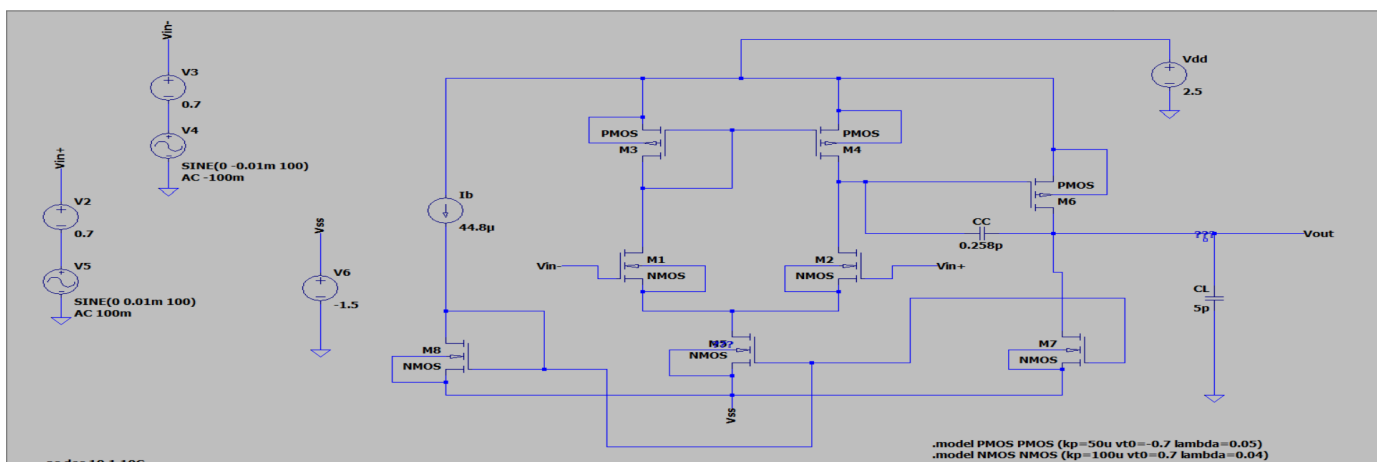So now we decrease the value of C_c to 0.258pf



Result :

DC operating point :


--- Operating Point ---					
V(n001) :	2.5	voltage			
V(n007) :	0.117364	voltage			
V(vout) :	0.436008	voltage			
V(n004) :	1.2208	voltage			
V(vin+) :	0.7	voltage			
V(n005) :	0	voltage	Ig (M7) :	0	device_current
V(vin-) :	0.7	voltage	Ib (M7) :	-1.94601e-12	device_current
V(n002) :	0	voltage	Is (M7) :	-0.00136009	device_current
V(n003) :	1.2208	voltage	Id (M4) :	-2.22188e-05	device_current
V(n006) :	-0.0979459	voltage	Ig (M4) :	-0	device_current
V(vss) :	-1.5	voltage	Ib (M4) :	1.2892e-12	device_current
Id (M1) :	2.22188e-05	device_current	Is (M4) :	2.22188e-05	device_current
Ig (M1) :	0	device_current	Id (M6) :	-0.00136009	device_current
Ib (M1) :	-1.32875e-12	device_current	Ig (M6) :	-0	device_current
Is (M1) :	-2.22188e-05	device_current	Ib (M6) :	2.07399e-12	device_current
Id (M2) :	2.22188e-05	device_current	Is (M6) :	0.00136009	device_current
Ig (M2) :	0	device_current	Id (M3) :	-2.22188e-05	device_current
Ib (M2) :	-1.32875e-12	device_current	Ig (M3) :	-0	device_current
Is (M2) :	-2.22188e-05	device_current	Ib (M3) :	1.2892e-12	device_current
Id (M5) :	4.44376e-05	device_current	Is (M3) :	2.22188e-05	device_current
Ig (M5) :	0	device_current	I (Cc) :	-2.02476e-25	device_current
Ib (M5) :	-1.41205e-12	device_current	I (C1) :	-2.18004e-24	device_current
Is (M5) :	-4.44376e-05	device_current	I (Ib) :	4.48e-05	device_current
Id (M8) :	4.48e-05	device_current	I (Vdd) :	-0.00144933	device_current
Ig (M8) :	0	device_current	I (V2) :	0	device_current
Ib (M8) :	-1.62736e-12	device_current	I (V3) :	0	device_current
Is (M8) :	-4.48e-05	device_current	I (V4) :	0	device_current
Id (M7) :	0.00136009	device_current	I (V5) :	0	device_current
			I (V6) :	0.00144933	device_current

Bode plot :

At Input common dc voltage 0.7 Volts



At Input common dc voltage 1.6 Volts

 

DC Gain (simulation):- 66.01 dB(for 0.7 volts) and 65.408 dB(for 1.6 volts)

Specifications(LTSpice)	Value(At 0.7v)	Value(At 1.6v)
DC Gain	1997.56	1862.08
Phase Margin	70.05	70.74
Gain Bandwidth Product	50.35 MHz	50.83 MHz

LT Spice (Output log) :

Semiconductor Device Operating Points:

--- MOSFET Transistors ---

Name:	m1	m2	m5	m8	m7	m4	m6	m3
Model:	nmos	nmos	nmos	nmos	nmos	pmos	pmos	pmos
Id:	2.30e-05	2.30e-05	4.59e-05	4.48e-05	1.38e-03	-2.30e-05	-1.38e-03	-2.30e-05
Vgs:	8.01e-01	8.01e-01	1.62e+00	1.62e+00	1.62e+00	-1.29e+00	-1.29e+00	-1.29e+00
Vds:	4.13e-01	4.13e-01	2.30e+00	1.62e+00	2.33e+00	-1.29e+00	-1.67e+00	-1.29e+00
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	7.00e-01	7.00e-01	7.00e-01	7.00e-01	7.00e-01	-7.00e-01	-7.00e-01	-7.00e-01
Vdsat:	1.01e-01	1.01e-01	9.17e-01	9.17e-01	9.17e-01	-5.89e-01	-5.89e-01	-5.89e-01
Gm:	4.53e-04	4.53e-04	1.00e-04	9.77e-05	3.01e-03	7.80e-05	4.69e-03	7.80e-05
Gds:	9.04e-07	9.04e-07	1.68e-06	1.68e-06	5.05e-05	1.08e-06	6.37e-05	1.08e-06
Gmb:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Chd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgdov:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgb:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgb:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00

END OF REPORT !!!